

$$1.53 \times 10^{-10}$$

27. Answer: D

For B and C, $V_x = 0$, due to the direction of the diodes.

Using potential divider rule for both A and D,

$$\text{A: } \frac{V_x - 0}{12 - 0} = \frac{2}{2 + 4} \Rightarrow V_x = 4 \text{ V}$$

$$\text{D: } \frac{V_x - 0}{12 - 0} = \frac{4}{2 + 4} \Rightarrow V_x = 8 \text{ V}$$

28. Answer: B