

$$12 - 0 = 2 + 4$$

28. Answer: B

When the LDR is moved into the dark, the resistance of the LDR increases greatly. Thus I_2 will increase, since the current going through the LDR will decrease greatly. The total resistance of the resistors will also increase, thus I_1 will decrease.