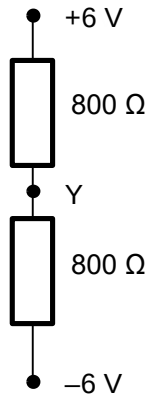


29. Answer: A

If we are to take the potential of any points of the circuit with reference to point X, i.e. $V_X = 0$ V, the potential difference across the resistors can be represented as follows:



Using the potential divider rule,

$$\frac{V_Y - (-6)}{6 - (-6)} = \frac{800}{1600}$$

$$\therefore V_Y = 0 \text{ V}$$

Since the potential at X and Y are the same, no current will flow from X to Y when the wire is attached from X to Y.