

25 $R = \frac{V}{I}$, R decreases for $V > 0.6 \text{ V}$

Answer: A

26 e.m.f. of battery = sum of p.d. across all resistors