

Answer: B

28 Total resistance in circuit $= \frac{1}{\frac{1}{6} + \frac{1}{6}} + 3 = 6\Omega$

$$\text{Current in circuit} = \frac{V}{R} = \frac{12}{6} = 2A$$

$$\text{Current through ammeter} = 1A$$

Answer: B

29 When P and Y are in series $I = 0.3A$ (given)