

Answer: C

- 26** When the resistance of the variable resistor is decreased, the current passing through the whole circuit increases.

Therefore, terminal p.d. will decrease, since $V = E - Ir$.

The power wasted in the cell is the power dissipated by the internal resistance, and it increases with the increase in current, since $P = I^2r$.

Answer: B

- 27** Since the cross sectional area is constant throughout, the number of free electrons