

Answer: C

- 28** In order to produce the smallest reading on the voltmeter, the total resistance across the thermistor and the LDR has to be as small as possible, based on potential divider rule.

Since the resistance of the thermistor and LDR decreases with increasing temperature and increasing brightness respectively, both brightness and temperature has to be high.

Answer: A