

19. Answer: B

When the ideal semiconductor diode is forward biased, current flows through the resistor and Ohm's law applies. When the diode is reverse biased, no current flows through the resistor.