

**25. Answer: A**

In full-wave rectifier,  $V_{\text{r.m.s.}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{224}{\sqrt{2}} = 158.4 \text{ V}$

r.m.s current,  $I_{\text{r.m.s.}} = \frac{158.4}{70.0} = 2.263 \text{ A}$

power to the resistor,  $P = I_{\text{r.m.s.}}^2 R = 2.263^2 \times 70.0 = 358 \text{ W}$