

26. Answer: B

$$\text{Peak output voltage} = \frac{180}{16} = 11.25 \text{ V}$$

$$V_{\text{r.m.s.}} = \frac{11.25}{\sqrt{2}} = 7.955 \text{ V}$$

$$\text{Using } P = \frac{V^2}{R},$$

$$R = \frac{V_{\text{r.m.s.}}^2}{P} = \frac{7.955^2}{32} = 1.978 \approx 2.0 \text{ } \Omega$$