

22. Answer: A

$$\text{Total e.m.f. of the battery} = 1.5 \times 3 = 4.5 \text{ V}$$

$$\text{Effective resistance } R_{\text{eff}} = \frac{0.6 \times 0.6}{0.6 + 0.6} = 0.3 \, \Omega$$

23. Answer: D