

No.	Answer	Solution
23	C	Below 2.0 V, the I - V graph would be that of an ohmic resistor of resistance 4.0 Ω . Beyond 2.0 V, there will be an additional constant current through the diode. Hence the graph will have the same gradient as the part below 2.0 V but raised by a constant amount.
24	D	When the variable resistor is set at zero, the e.m.f. of 12 V is applied across the 1.0 k Ω resistor hence $V = 12$ V.