

24	D	When the variable resistor is set at zero, the e.m.f. of 12 V is applied across the 1.0 kΩ resistor hence $V = 12$ V. When the variable resistor is set at 1.0 kΩ, $V = \frac{1.0}{1.0 + 0.50} \times 12 = 8.0 \text{ V}$
25	B	$\left[5.0 \times 10^{-3} - (-5.0 \times 10^{-3}) \right] (2.0 \times 10^{-2})$