

		$t = 1.6 \times 10^{-8} \text{ s}$
20	B	Current = $\frac{6.0}{11 + 1.0} = 0.50 \text{ A}$ New current = $\frac{6.0 + 6.0}{11 + 1.0 + 1.0} = 0.923 \text{ A}$ Ratio = $\frac{0.923}{0.50} = 1.846$ Therefore the increase in ammeter reading is by a factor of less than 2.
21	A	$\rho(2L) = \rho(L)$