

		Therefore the increase in ammeter reading is by a factor of less than 2.
21	A	$\frac{\rho(3L)}{A} + \frac{\rho(L)}{2A} = 84.0 \ \Omega$ $\frac{\rho L}{A} = 24.0 \ \Omega$ Therefore resistance of resistor Q = $\frac{\rho L}{2A} = 12.0 \ \Omega$
22	B	As the resistance of the variable resistor increases, the current