

|    |   |                                                                                                                                                  |
|----|---|--------------------------------------------------------------------------------------------------------------------------------------------------|
|    |   | 2A                                                                                                                                               |
| 22 | B | <p>As the resistance of the variable resistor increases, the current decreases.</p> <p>Terminal potential difference <math>V = E - Ir</math></p> |

| No. | Answer | Solution                                                                                                                                             |
|-----|--------|------------------------------------------------------------------------------------------------------------------------------------------------------|
|     |        | Electromotive force of cell remains constant.<br>Internal resistance of cell remains constant.<br>Therefore terminal potential difference increases. |
| 22  | B      | Option A: Total resistance $= R$                                                                                                                     |