

		4
22	A	The sum of the p.d. across the resistor and the thermistor is 3.0 V. The same current flows through the resistor and the thermistor, since they are connected in series. By examining the graph, when the current flowing through the resistor and the thermistor is 0.10 A, the p.d. across the resistor is 1.0 V and the p.d. across the thermistor is 2.0 V. The sum of the p.d.'s is 3.0 V, which is equal to the e.m.f. of the battery connected to the circuit.
23	C	In order for the filament lamp to glow more brightly, the p.d. across the lamp