

27**B**

Use $\frac{V_s}{V_p} = \frac{I_p}{I_s}$, where $\frac{V_s}{V_p} = \text{gradient of graph} = \frac{17}{2.0}$,

Secondary current

$$\begin{aligned} I_s &= \frac{V_p}{V_s} \times I_p \\ &= \frac{2.0}{17} \times 0.32 \\ &= 0.0376 \text{ A} \\ &= 38 \text{ mA} \end{aligned}$$