

6(a)(i),
(ii)

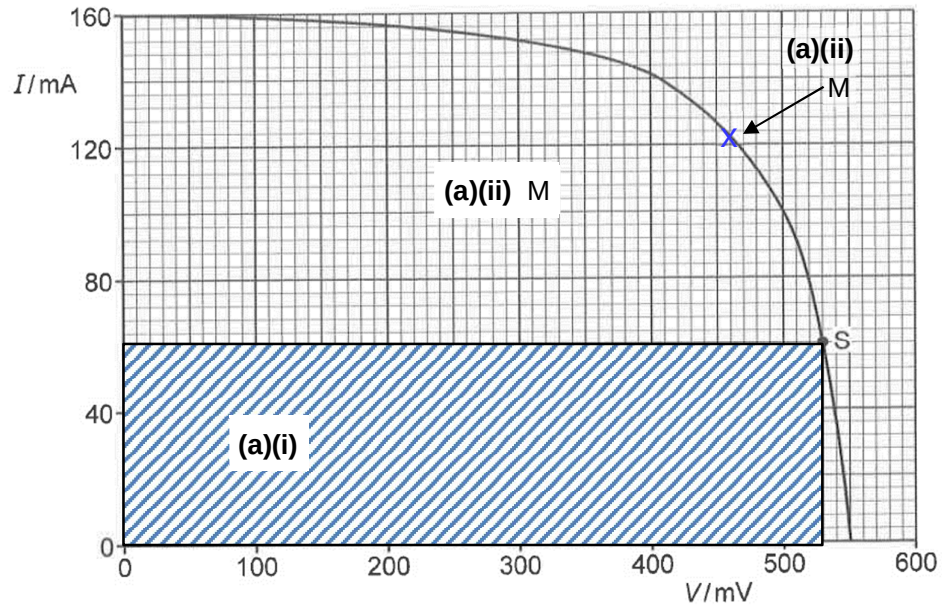


Fig. 6.2

No.	Solution
6(b)(i)	From Fig. 6.2, $V = 500 \text{ mV}$ when $I = 500 \text{ mA}$, $R = \frac{V}{I}$ $= \frac{500 \times 10^{-3}}{100 \times 10^{-3}}$ $= 5.0 \, \Omega$
6(b)(ii)	Power dissipated in resistor R $P = I^2 R$ $= (100 \times 10^{-3})^2 \times 5.0$ $= 0.050 \text{ W}$
6(b)(iii)	From Fig. 6.2, $V = 550 \text{ mV}$ when $I = 0 \text{ mA}$, i.e. e.m.f. of solar cell, $E = 550 \text{ mV}$ When $I = 500 \text{ mA}$, $E = V + Ir$ $r = \frac{E - V}{I}$ $= \frac{(550 - 500) \times 10^{-3}}{100 \times 10^{-3}}$ $= 0.50 \, \Omega$
7(a)	similarity: