

		$R_Q = 0.25$
22	B	Potential difference across wire, $V_{AB} = 0.84 \times 14.3$ $= 12.012 \text{ V}$ E.m.f. of cell, $E = \frac{0.65}{0.84} \times 12.012$ $= 9.295$ $= 9.3 \text{ V}$
23	C	Two parallel current-carrying wires with currents in the same direction will