

			$\approx 2.7 \times 10^{-3} \text{ s}$
	19	A	As the resistance of R is gradually decreased from its maximum value, the total resistance of the circuit is decreased causing the current in the circuit to increase. Hence, the reading on the ammeter increases. However, the p.d. across the variable resistor R decreases, causing the reading on the voltmeter to decrease.
	20	C	Let resistance of variable resistor be R , p.d. across lamp be V