

Qn	Answer	Solution
22	A	When temperature of thermistor is 50°C, $R_T = 1.00 \text{ k}\Omega$ By potential divider principle, $V = \frac{1.00}{1.00 + 5.00} \times 20$ $= 3.33$ $\approx 3.3 \text{ V}$
23	D	