

Qn	Answer	Solution
22	D	X is connected to the negative terminal of cell E. Hence, X must be connected to the either P or R of the potentiometer circuit to be balanced by the p.d. across part of the resistance wire. If X is connected to P, Y must be connected to Q. No such option. If X is connected to R, and Y is connected to Q, the e.m.f. of cell E might not be balanced by the p.d. V_{QR} across QR because there is insufficient information in the question. Option B is incorrect. If X is connected to R, Y must be connected to P. Option D is correct.
23	C	An increase in light intensity causes the resistance of an LDR to decrease.