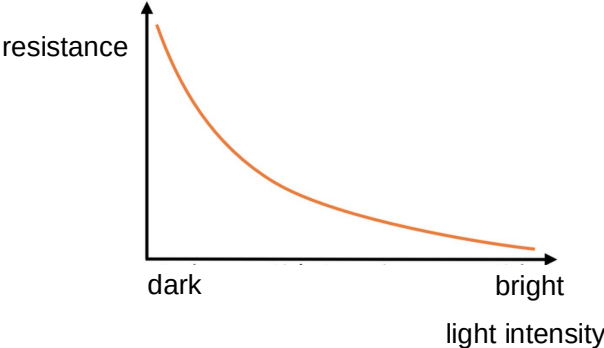


		If X is connected to R, Y must be connected to P. Option D is correct.
23	C	An increase in light intensity causes the resistance of an LDR to decrease. So, in dark conditions the resistance of an LDR is high, and in bright light conditions the resistance of an LDR is low. The graph shows the variation with light intensity of the resistance of an LDR.  When the intensity of light incident on the LDR is large, the resistance of the LDR is low, but the resistance of the fixed resistor remains constant. Hence, the combined resistance of the two resistors R is dominated by the resistance of the fixed resistor and remains relatively constant in bright light condition.
24	A	