

		19
19	D	Applying Ohm's law , $E = I(R + r)$ $E = 0.5(4.0 + r)$ $E = 0.25(10 + r)$ Solving, $r = 2 \, \Omega, E = 3 \, \text{V}$
20	A	Option A: Correct