

		$I = 2\text{ A}, L = 5\text{ V}$
20	A	Option A: Correct

Qn	Answer	Solution
		Option B: Incorrect Lamps have their own switches and thus cannot be switched on together using a single switch. Option C: Incorrect The lamps are in series and thus the voltage across each of them is 3 V and not 12 V. Option D: Incorrect The voltage across each lamp is only 6 V.
21	A	When the variable resistor is set to $0\ \Omega$, the voltmeter reads 6.0 V