

		The voltage across each lamp is only 0 V.
21	A	When the variable resistor is set to $0\ \Omega$, the voltmeter reads 6.0 V. When the variable resistor is set to $12\ \Omega$, by potential divider principle, $V = \frac{3.0}{12 + 3.0} \times 6.0 = 1.2\ \text{V} .$ Thus, the voltage decreases.
22	A	When the temperature of light dependent resistor increases, its resistance