

		Thus, the voltage decreases.
22	A	When the temperature of light-dependent resistor increases, its resistance decreases. By potential divider principle, p.d. across LDR decreases and p.d. across variable resistor increases.
23	D	