

		$\frac{1}{2}$
21	A	Using potential divider principle, $\text{p.d across } 2.0 \, \Omega \text{ resistor} = \frac{2.0}{2.0 + 1.0} \times 0.60 = 0.40 \, \text{V}$ Polarity connected to Q is positive and P is negative.
22	A	When the temperature of the thermistor rises, its resistance decreases. The