

		Polarity connected to Q is positive and P is negative.
22	A	When the temperature of the thermistor rises, its resistance decreases. The overall resistance in the circuit decreases and the current flowing in the circuit increases. Hence A_1 increases. The resistor beside the ammeter and thermistor are arranged in parallel $\Rightarrow$ the potential difference across both resistor and the thermistor is the same. Since the resistance of thermistor decreases, the current flowing through it is larger. $\Rightarrow$ current A_2 decreases.
23	C	If the negative ion were to move in a straight line passes through holes D and