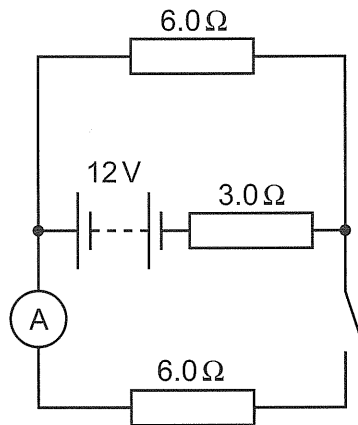


- 28** In the circuit, the battery has an e.m.f. of 12 V and an internal resistance of $3.0\ \Omega$. The ammeter has negligible resistance.



The switch is closed.

What is the reading on the ammeter?

- A** 0.50 A **B** 1.0 A **C** 1.3 A **D** 2.0 A